

4bit full adder/subtractor

Projetos de Hardware e Interfaciamento


Danilo Nicioka - 201906840035
Pedro Rendeiro - 201906840032

Project

Requirements


- **1bit full adder** from logic gates using std_logic_1164;
- From the 1bit adder, build a top-level file that implements a **4bit adder**;
- The 4bit adder must be configured to allow **sum or subtraction** operations;

Hierarchy

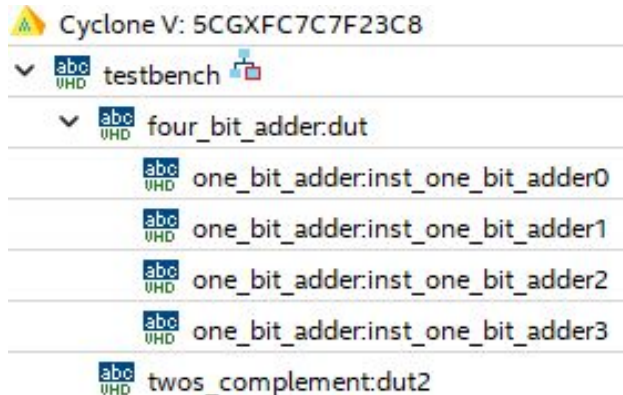


Logic gates

Testbench

 


Logic gates

4bit adder/subtractor

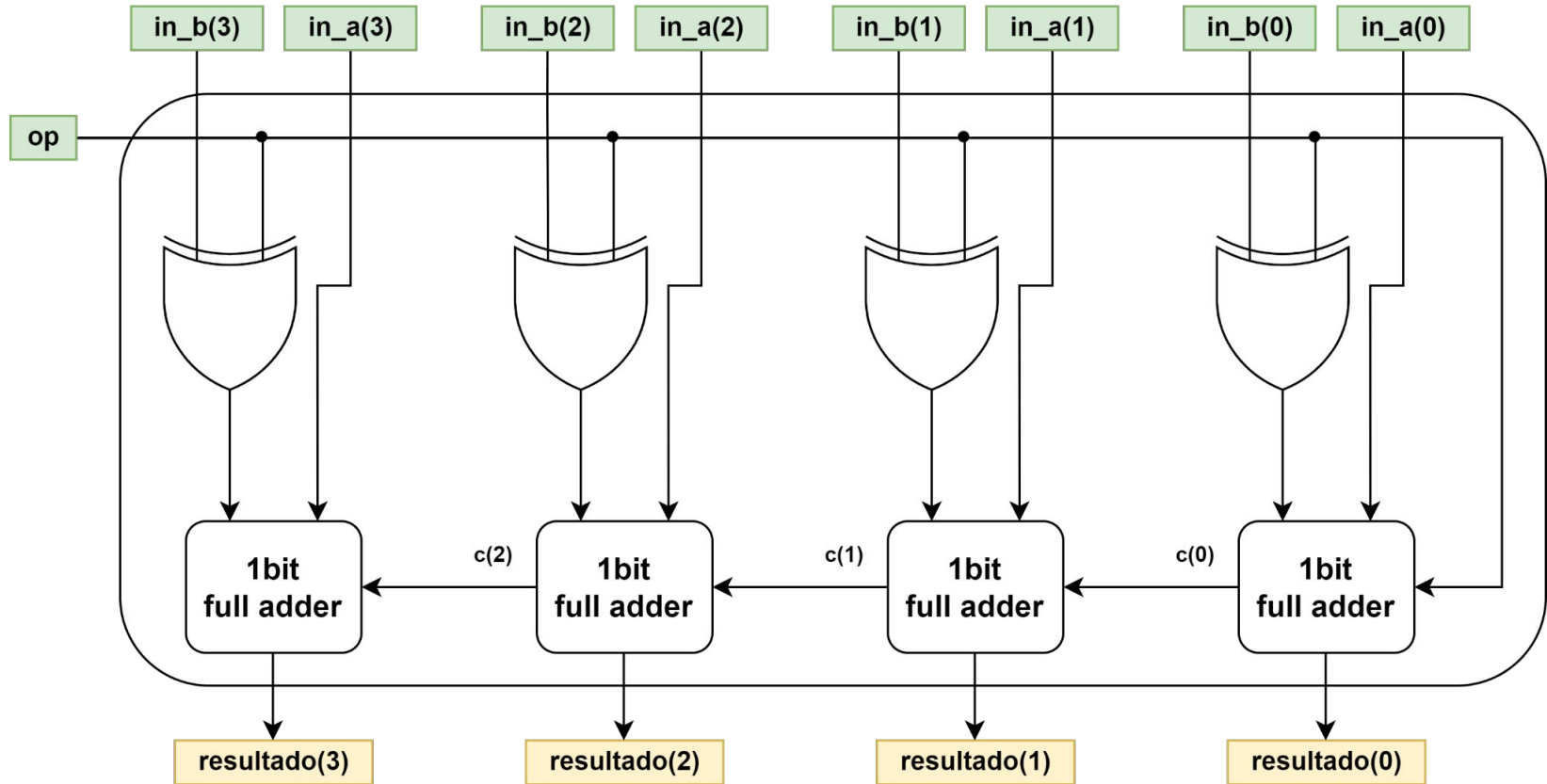


Logic gates

1bit full adder

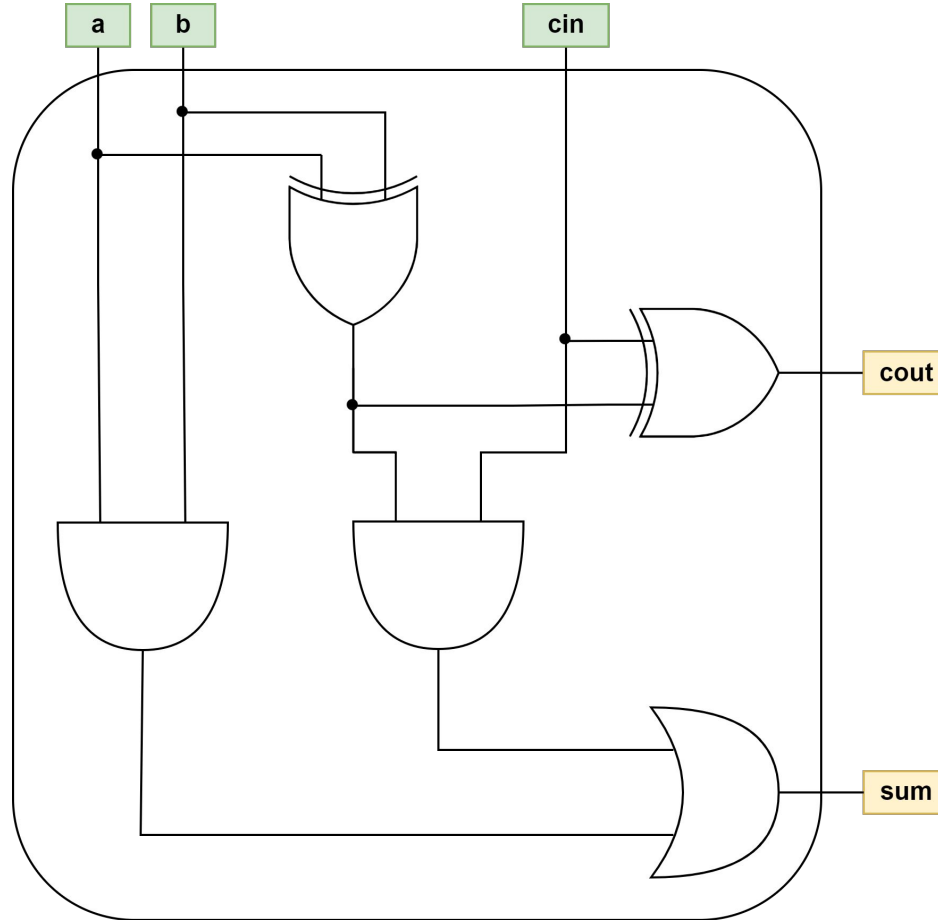


Logic gates

2's complement to unsigned

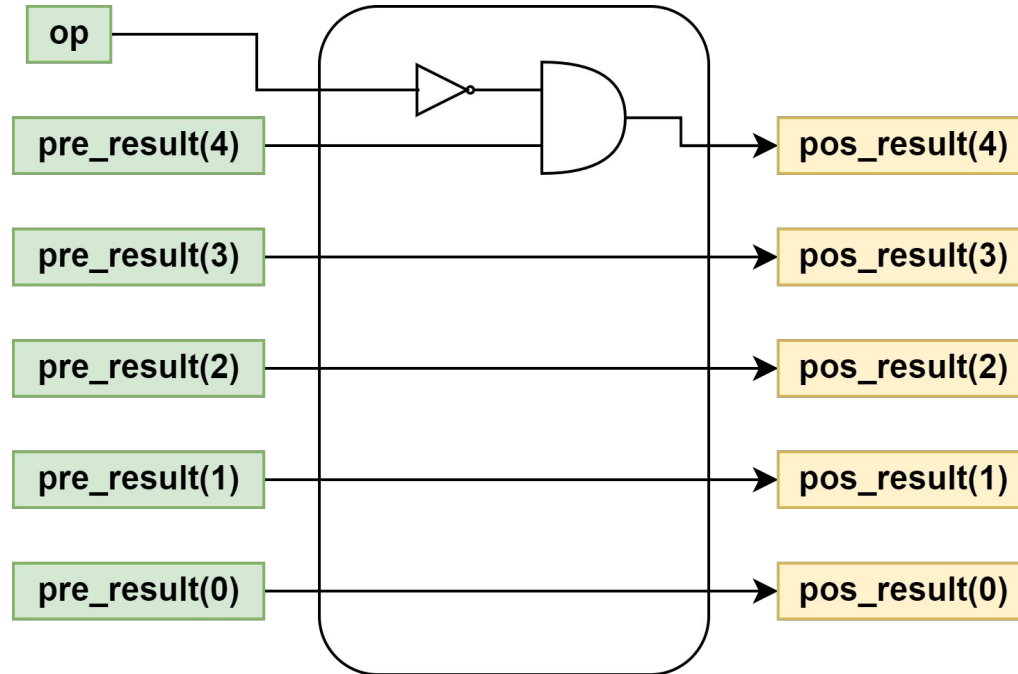


Register transfer level

4bit adder/subtractor

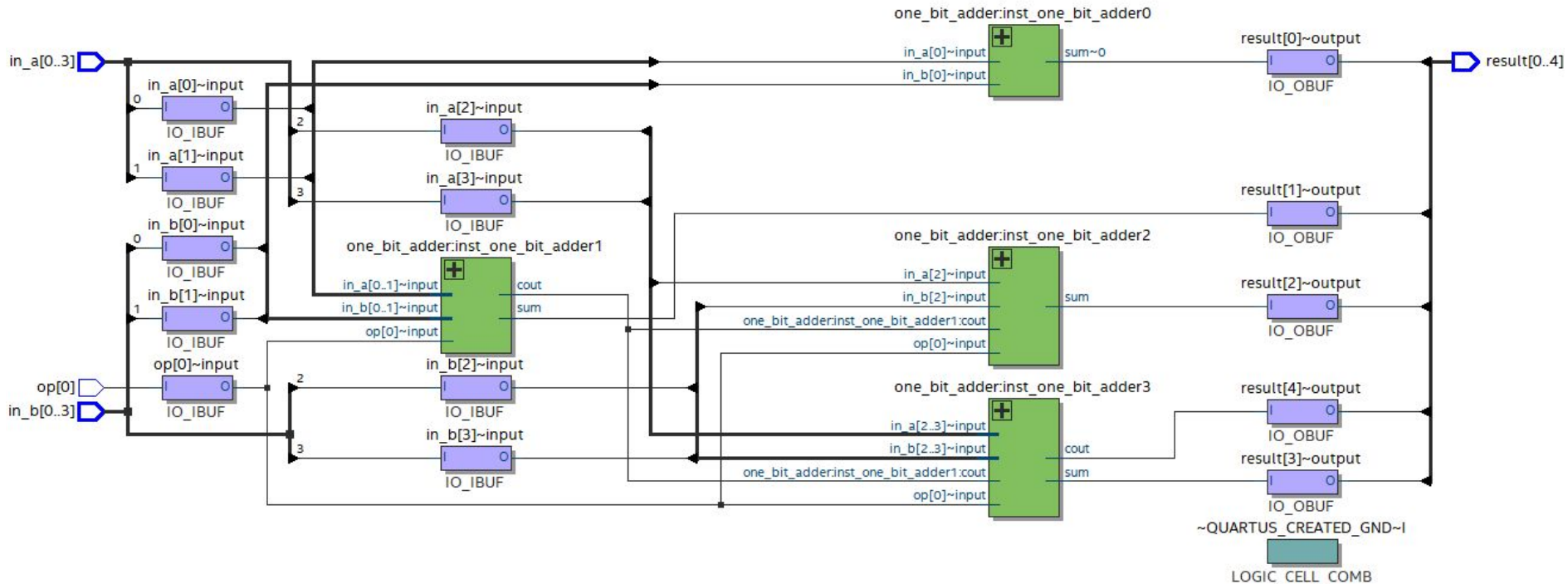


Register transfer level

2's complement to unsigned

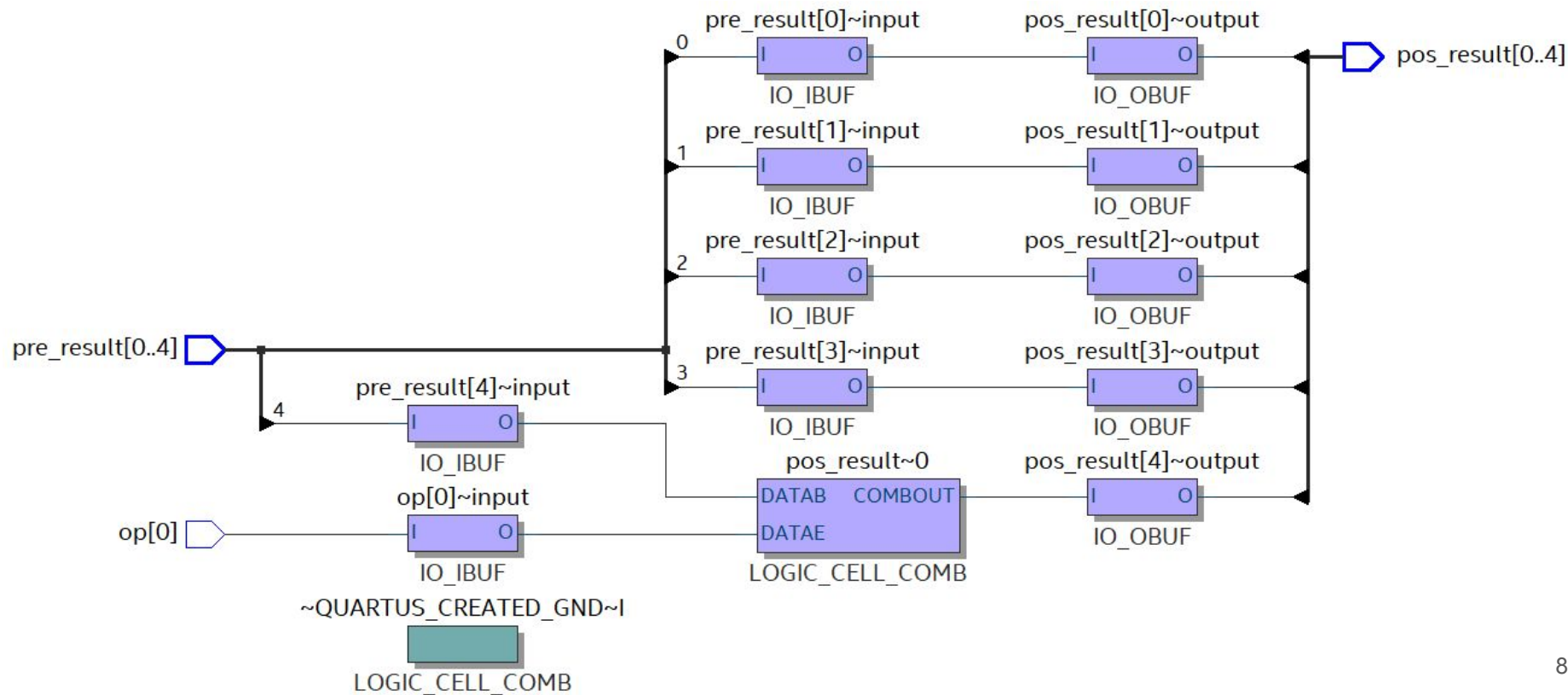

Simulation

Modelsim

 


sign_a, sign_b and sign_final_result as unsigned



sign_a, sign_b and sign_final_result as binary

Simulation

Modelsim

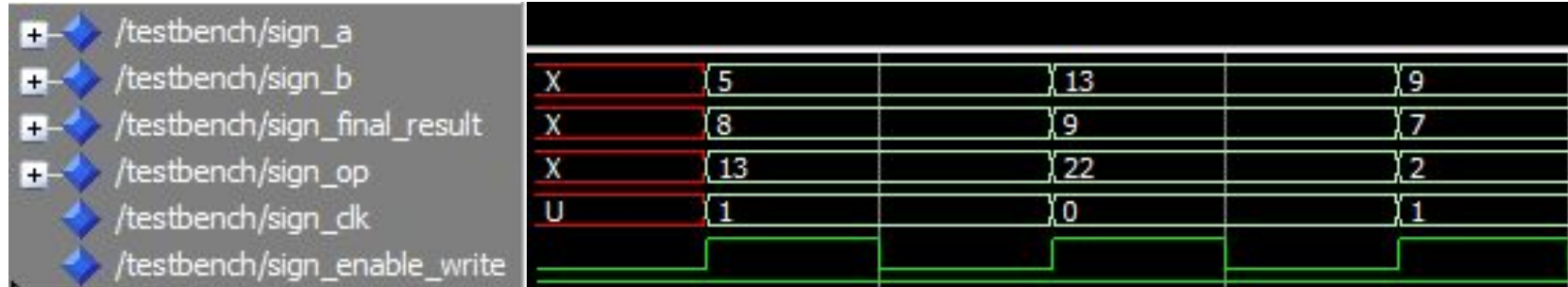

Limitation: the 2nd operator (`sign_b`) must be smaller than the 1st (`sign_a`).